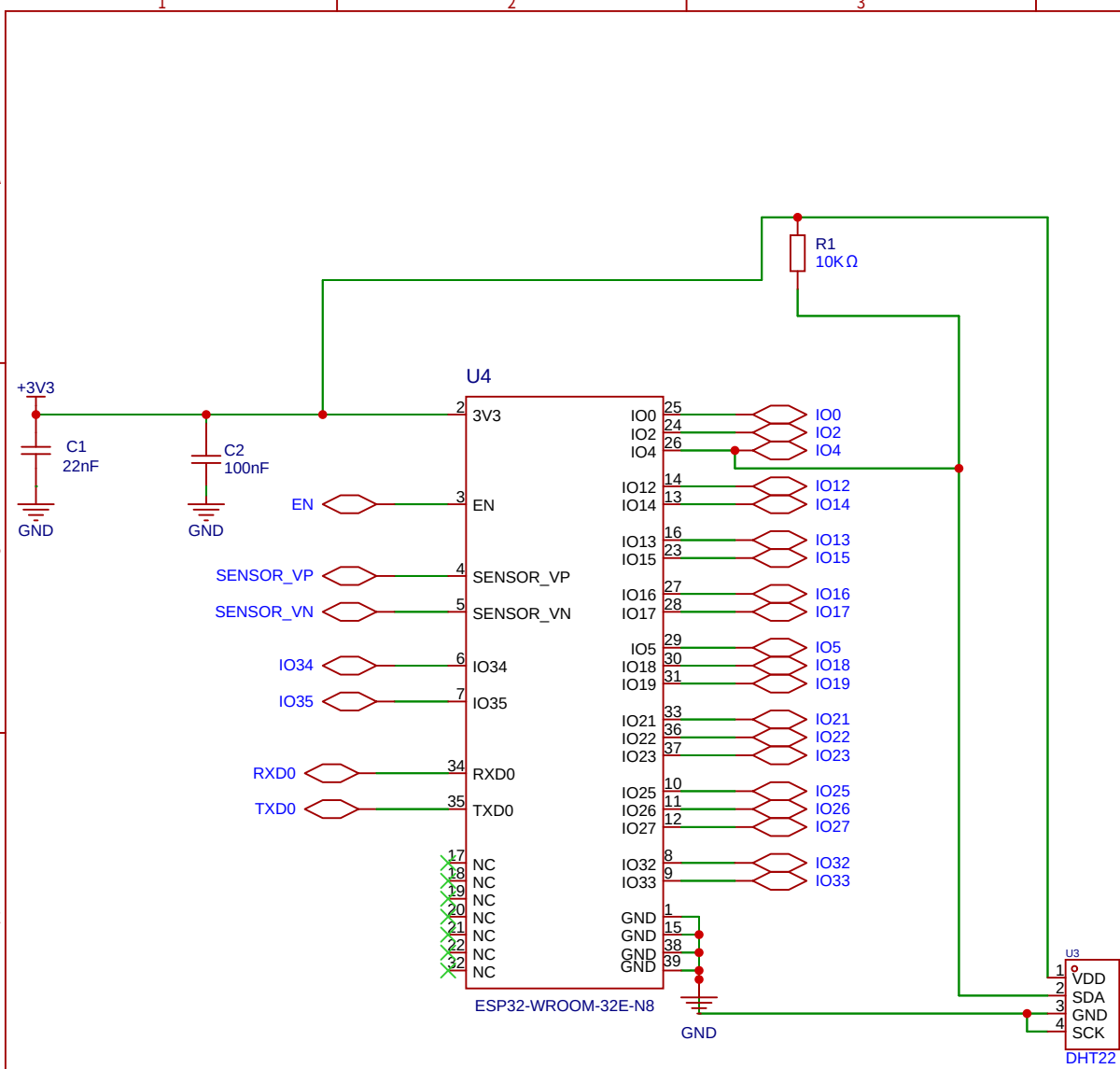




Component	Quantity	Use
ESP32-WROOM-32E-N8	1	The Main microcontroller board
DHT22 Sensor	1	The Temperature and humidity sensing module
10k Ω Resistor	1	A Pull-up resistor for DATA line
C1 - 22nF Capacitor	1	A decoupling capacitor for power supply
C1 - 100nF Capacitor	1	A decoupling capacitor for power supply
3.3V Power Supply	1	Powers the DHT22 Sensor
Jumper Wires	4	Circuit connections

Schematic	3. ESP32/DHT22 Schematic		Create at	2026-05-11
			Update at	2026-05-15
Board			Page	ESP32/DHT22 Schematic Connection
Drawn		Lab Exercise Schematics with ESP32		
Reviewed				
		Version	Size	Page 1 Total 1
EasyEDA		V1.0	A4	EasyEDA.com